

# Electronics Design Principles

## Scaled Adder

Name: Rajkaran Singh Grewal

Student No: 8882386

Student Email: rgrewal2386@conestogac.on.ca

**Object:** Build a scaled adder that is inverting input R1 will be amplified by 10 and the other R2 by 5.


Use 10 Kohm resistor for the input resistor R1 and calculate Rf. Use the same Rf to calculate R2.

Show your design in using MultiSim in your pre-lab.

Prepare a table for measurement in advance to prove that your circuit work by comparing your calculated values with the actual values.


**Equipment:** Oscilloscope, power supply, function generator, resistors, LM348M op amp, wires, breadboard.

## Schematic:

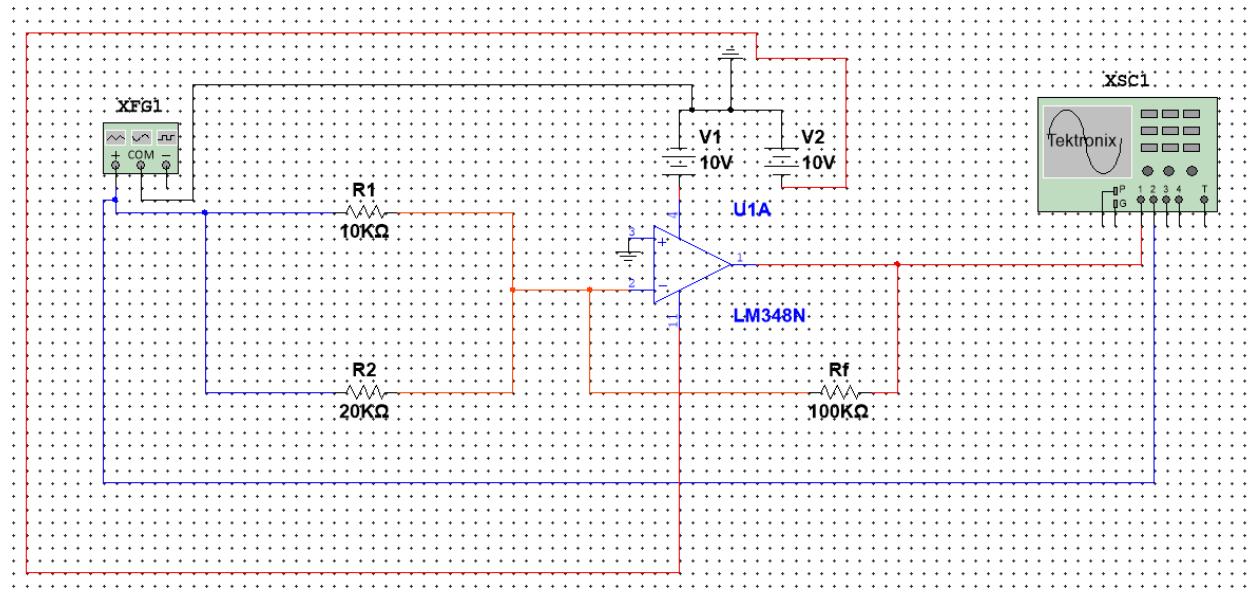

## Output:

Case 1:  $V_{pp} = 1.0V$

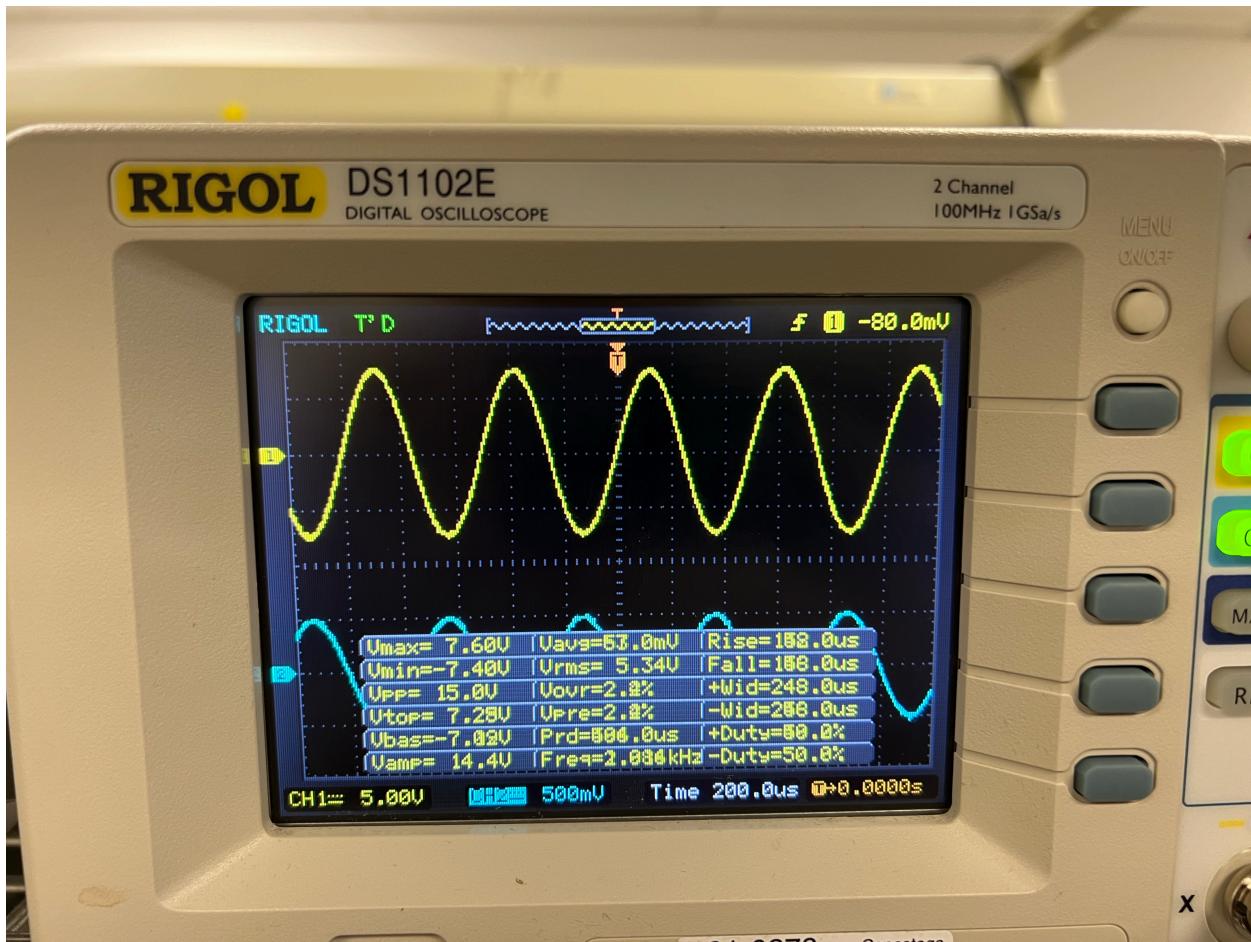


### Real Values

Type	CH1	CH2
$V_{max}$	7.6V	500mV
$V_{min}$	-7.4V	-500mV
$V_{pp}$	15V	1V
$V_{top}$	7.25V	463mV
$V_{base}$	-7.02V	-477mV
Period	500.0us	500.0us
Frequency	2kHz	2.016kHz

Multisim Value

Type	CH1	CH2
Pk-Pk	14.9V	999mV
Min	-7.49V	-499mV
Max	7.5V	499V

Case 2: V<sub>pp</sub> = 500mV

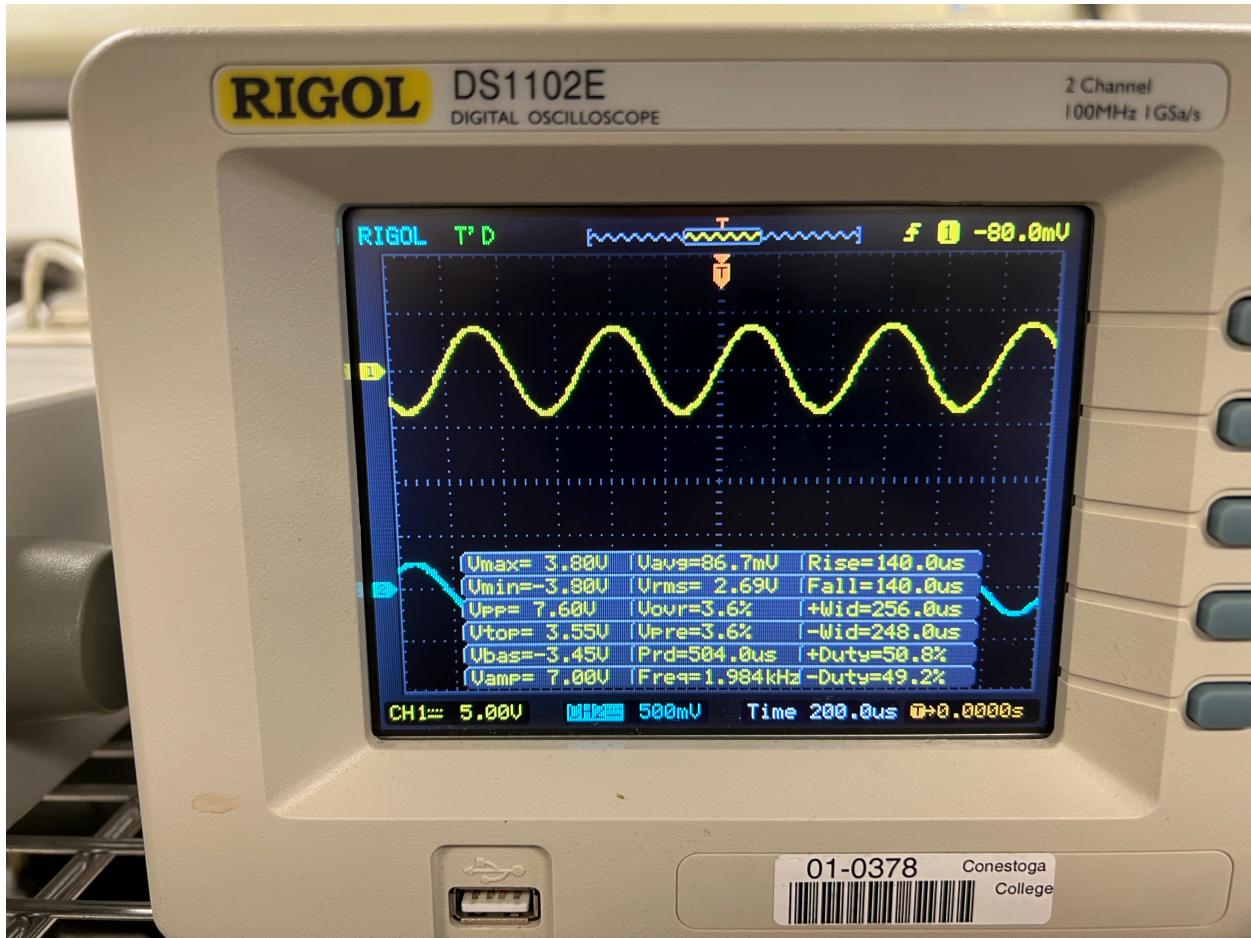

Real Value


Type	CH1	CH2
V <sub>max</sub>	3.8V	240mV
V <sub>min</sub>	-3.8V	-260mV
V <sub>pp</sub>	7.6V	500mV
V <sub>top</sub>	3.55V	216mV

Type	CH1	CH2
V <sub>base</sub>	-3.45V	-235mV
Period	500.0us	500.0us
Frequency	2kHz	2kHz

Multisim Value

Type	CH1	CH2
Pk-Pk	7.47V	499mV
Min	-3.73V	-249V
Max	3.74V	249V

Case 3: V<sub>pp</sub> = 750mV

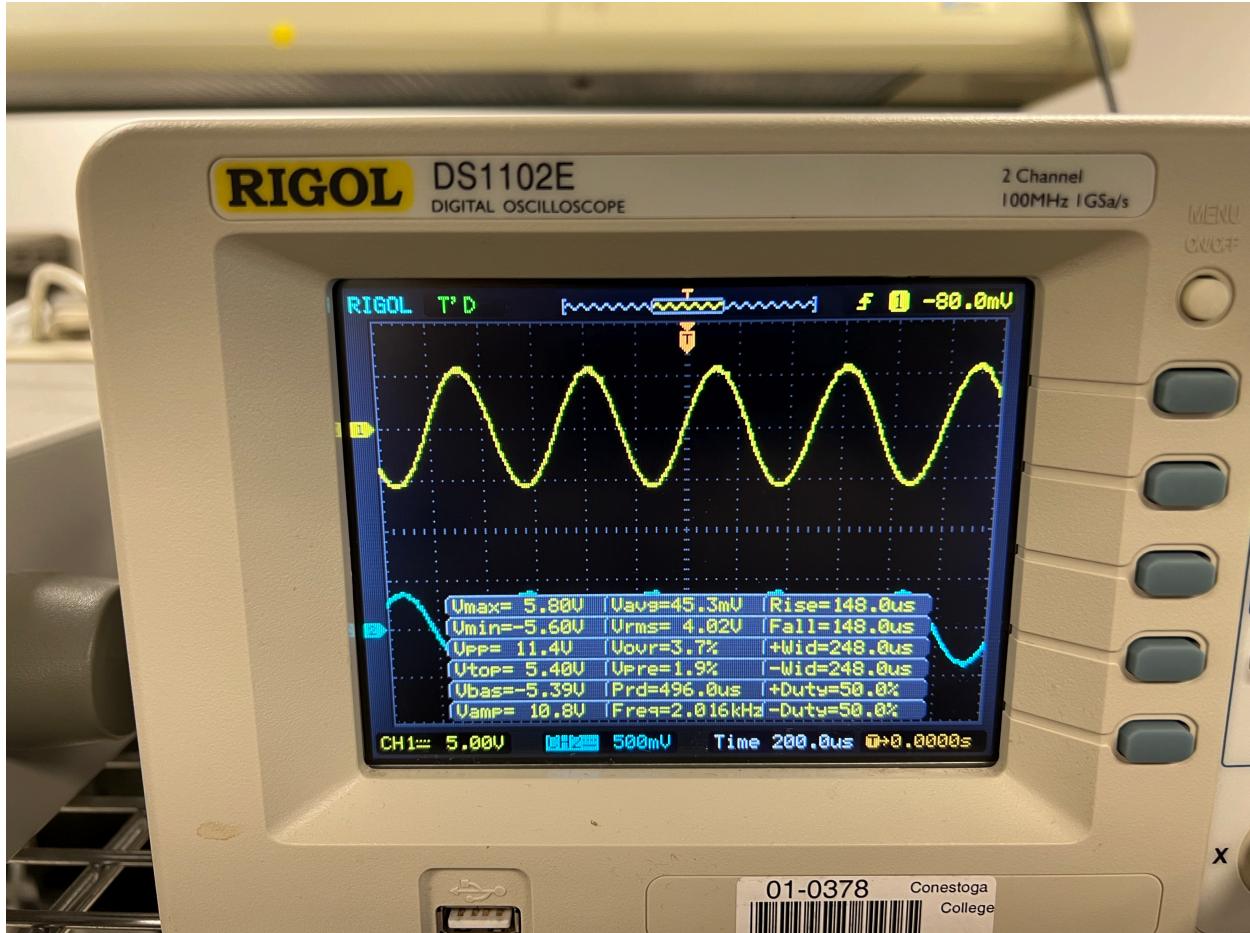

Real Value


Type	CH1	CH2
V <sub>max</sub>	5.8V	380mV
V <sub>min</sub>	-5.6V	-400mV
V <sub>pp</sub>	11.4V	780V
V <sub>top</sub>	5.4V	346mV
V <sub>base</sub>	-5.39V	-350mV

Multisim Value

Type	CH1	CH2
Pk-Pk	11.2V	748mV
Min	-5.61V	-374mV

Type	CH1	CH2
Max	5.62V	374V

Case 4: Vpp = 250 mV

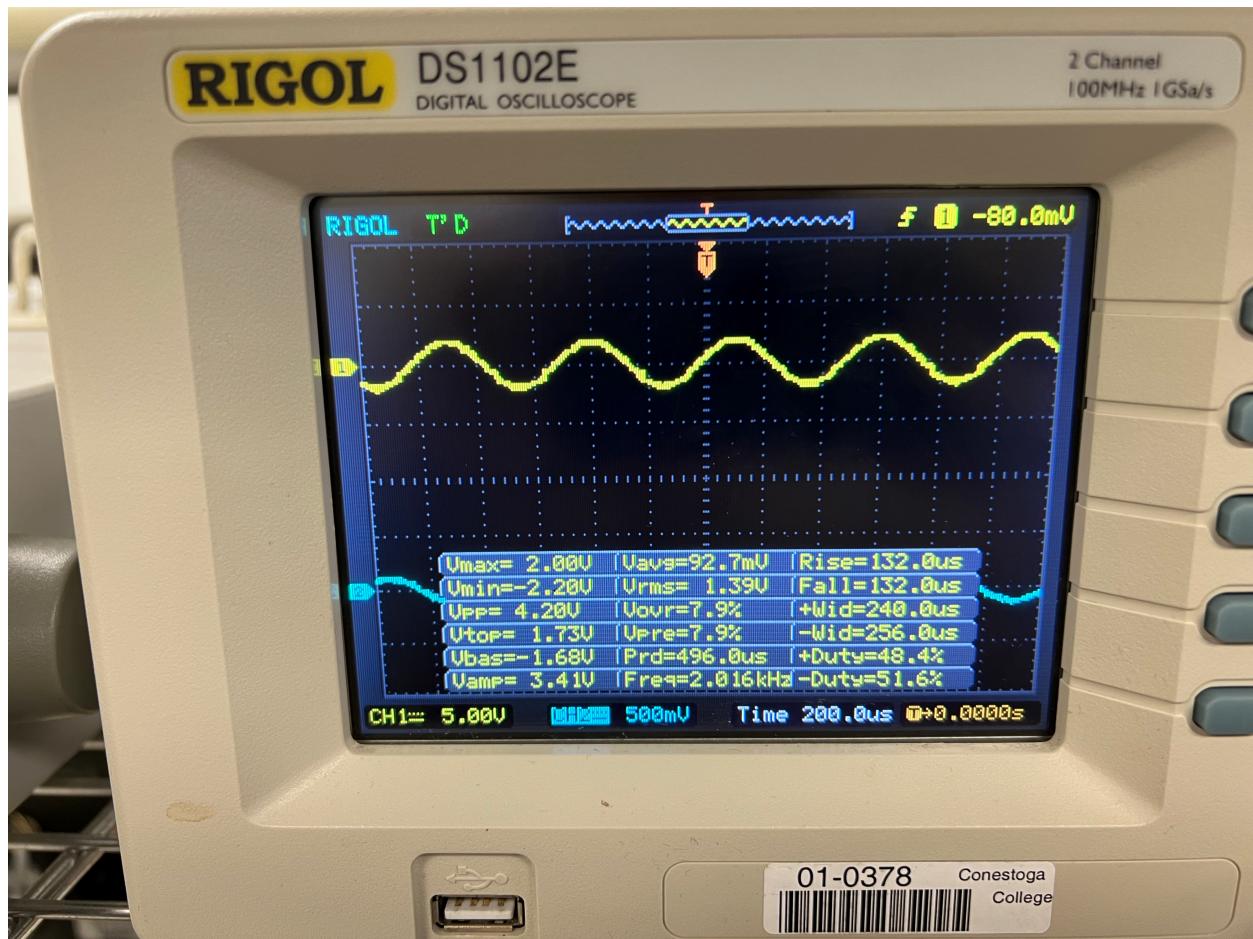


Real Value

Type	CH1	CH2
<b>V<sub>max</sub></b>	2V	120mV
<b>V<sub>min</sub></b>	-2.2V	-140mV
<b>V<sub>pp</sub></b>	4.2V	260mV
<b>V<sub>top</sub></b>	1.73V	88.4mV
<b>V<sub>base</sub></b>	-1.68V	-109mV

Multisim Value

Type	CH1	CH2
<b>Pk-Pk</b>	3.75V	250mV
<b>Min</b>	-1.87V	-125mV
<b>Max</b>	1.88V	125mV

Case 5:  $V_{pp} = 100$  mV

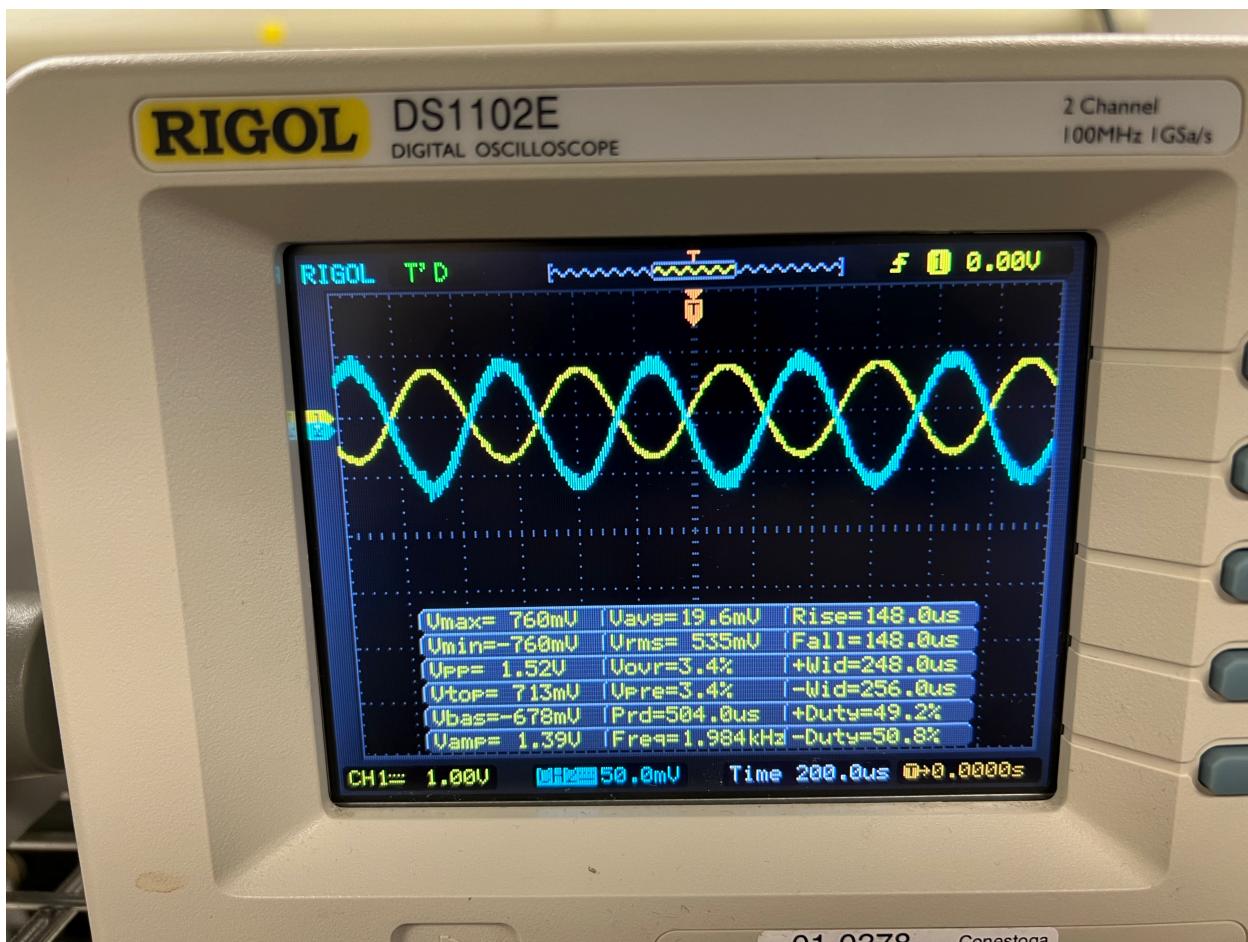

#### Real Value

Type	CH1	CH2
$V_{max}$	760mV	58mV
$V_{min}$	-760mV	-56V
$V_{pp}$	1.52V	114mV
$V_{top}$	713V	50.5mV
$V_{base}$	-678V	-48.8mV

#### Multisim Value

Type	CH1	CH2
Pk-Pk	1.5V	99.9mV

Type	CH1	CH2
Min	-746mV	-49.9mV
Max	752mV	49.9mV

## Input:

- Case 1:  $V_{pp} = 1.0V$
- Case 2:  $V_{pp} = 500mV$
- Case 3:  $V_{pp} = 750mV$
- Case 4:  $V_{pp} = 250mV$
- Case 5:  $V_{pp} = 100mV$

## Observations:

From the observation we can see that the  $V_{out}$  will remain the same even if the  $V_{in}$  is changed and the gain will always be 15 has the  $V_{in}$  is the same for both resistors and the gain is 10 and 5 which added together we get 15.

## Calculations:

$$R_f = - R_i \cdot A_{cl(l)1} = - 10K \text{ ohm} * 10 = - 100K \text{ ohm}$$

$$R_{i2} = - R_f / A_{cl(l)2} = - (-100K \text{ ohm}) / 5 = 20K \text{ ohm}$$

Case 1:

$$A_{cl(l)1} = - R_f / R_i$$

$$A_{cl(l)1} = - 100K / 10K = 10$$

$$A_{cl(l)2} = - 100K / 20K = 5$$

$$V_{out} = V_{in} \times A_{cl(l)1} + V_{in} \times A_{cl(l)2}$$

$$V_{out} = 1V \times 10 + 1V \times 5$$

$$V_{out} = 10V + 5V = 15V$$

Case 2:

$$A_{cl(l)1} = - R_f / R_i$$

$$A_{cl(l)1} = - 100K / 10K = 10$$

$$A_{cl(l)2} = - 100K / 20K = 5$$

$$V_{out} = V_{in} \times A_{cl(l)1} + V_{in} \times A_{cl(l)2}$$

$$V_{out} = 500mV \times 10 + 500mV \times 5$$

$$V_{out} = 5V + 2.5V = 7.5V$$

Case 3:

$$A_{cl(l)1} = - R_f / R_i$$

$$A_{cl(l)1} = - 100K / 10K = 10$$

$$A_{cl(l)2} = - 100K / 20K = 5$$

$$V_{out} = V_{in} \times A_{cl(l)1} + V_{in} \times A_{cl(l)2}$$

$$V_{out} = 750mV \times 10 + 750mV \times 5$$

$$V_{out} = 7.5V + 3.75V = 11.25V$$

Case 4:

$$A_{cl(l)} = - R_f/R_i$$

$$A_{cl(l)} = - 100K/10K = 10$$

$$A_{cl(l)} = - 100K/20K = 5$$

$$V_{out} = V_{in} \times A_{cl(l)} + V_{in} \times A_{cl(l)}^2$$

$$V_{out} = 250mV \times 10 + 250mV \times 5$$

$$V_{out} = 2.5V + 1.25V = 3.75V$$

Case 5:

$$A_{cl(l)} = - R_f/R_i$$

$$A_{cl(l)} = - 100K/10K = 10$$

$$A_{cl(l)} = - 100K/20K = 5$$

$$V_{out} = V_{in} \times A_{cl(l)} + V_{in} \times A_{cl(l)}^2$$

$$V_{out} = 100mV \times 10 + 100mV \times 5$$

$$V_{out} = 1V + 500mV = 1.5V$$

## Theory Vs Practical:

If we look at the values from multisim and the actual values from the oscilloscope we can see that the values we get in practical the lower the Vpp the function generator tends to overshoot, while the higher the Vpp the more the values remain the same. However in multisim the values are usually less than the actual values we get from the function generator.

## Conclusions:

We can finally conclude that if the Vin is same for both resistors than the gain will always be 15 and the output will amplify by 15. We used multiple different Vin and the results can be said to be similar to the multisim and the one we calculated using the formula.