

# Electronics Design Principles

## Differential Amplifier and Instrumentational Amplifier

Name: Rajkaran Singh Grewal

Student No: 8882386


Student Email: rgrewal2386@conestogac.on.ca

**Object:** Design and build an instrumental amplifier using an identical R values for all 7 resistors.

Build a differential amplifier first to test out your circuits before connecting to the rest.

**Equipment:** Oscilloscope, power supply, function generator, resistors, LM348M op amp, wires, breadboard.

### Schematic:


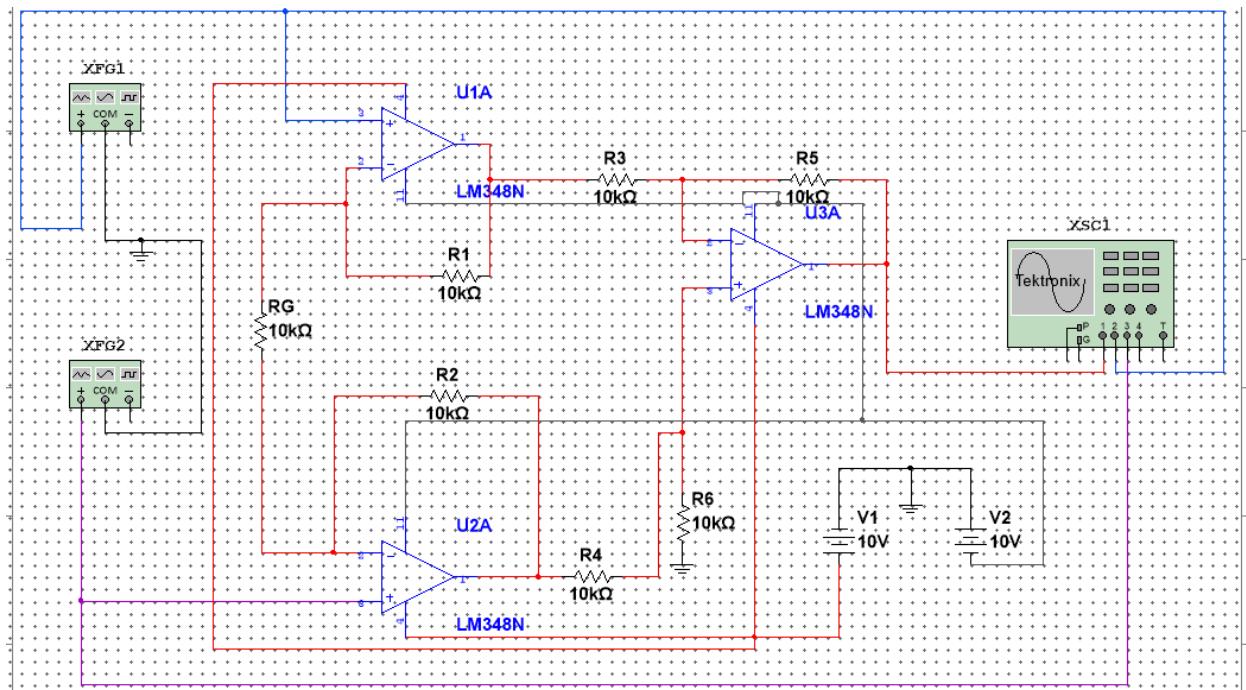


## Output:

Case 1:

CH1: 2 Vpp

CH2: 1 Vpp

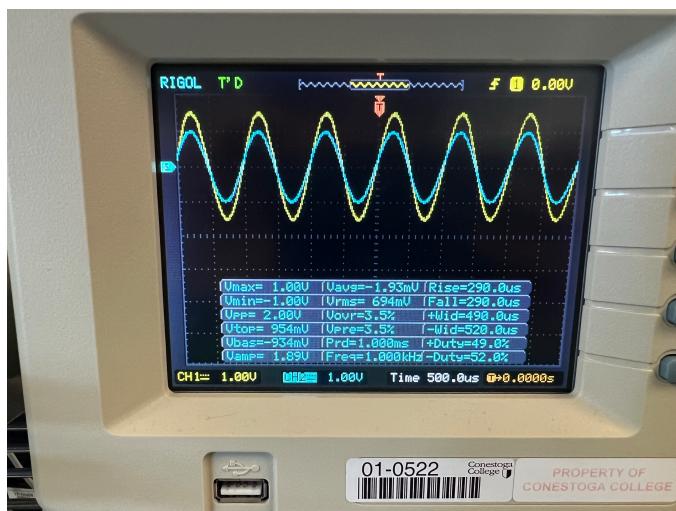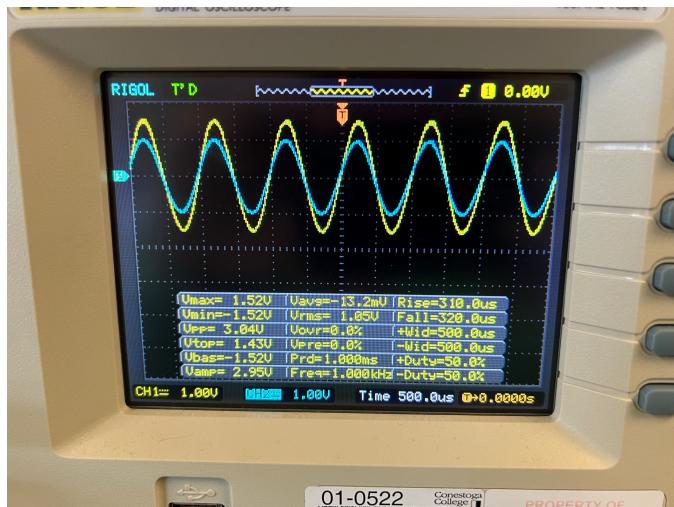

Real Values

Type	CH1	CH2
V <sub>max</sub>	1.52V	1V
V <sub>min</sub>	-1.52V	-1V
V <sub>pp</sub>	3.04V	2V


Multisim Value

Type	CH1	CH2
Max	1.5V	1V
Min	-1.5V	-1mV
Pk-Pk	3V	2mV

Case 2:

CH1: 5 Vpp

CH2: 2 Vpp

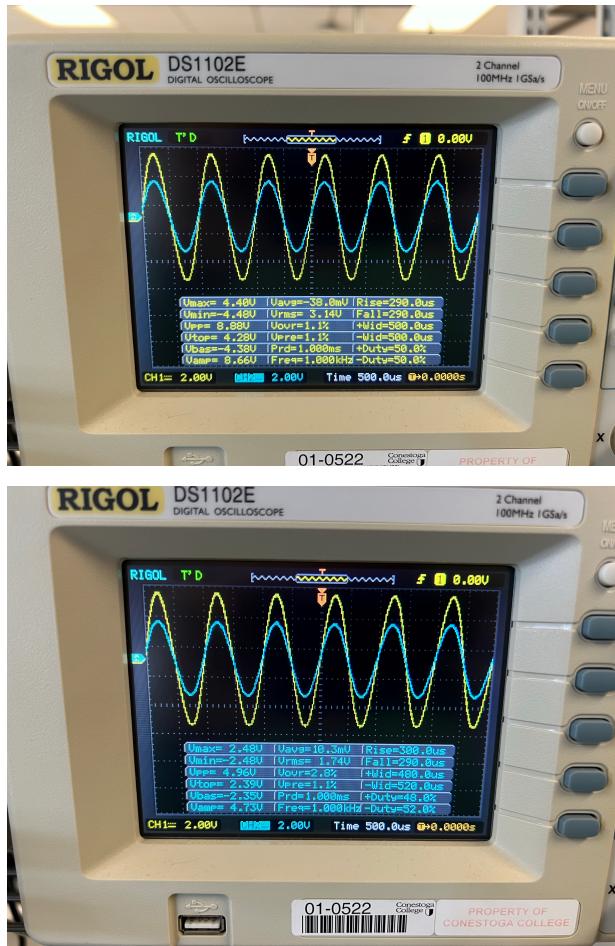

Real Value



Type	CH1	CH2
V <sub>max</sub>	4.4V	2.48V
V <sub>min</sub>	-4.48V	-2.48mV
V <sub>pp</sub>	8.88V	4.96V

## Multisim Value

Type	CH1	CH2
Max	-4.5V	2.5V
Min	-4.5V	-2.5V
Pk-Pk	9V	5V

Case 3:

CH1: 5 Vpp  
CH2: 1 Vpp

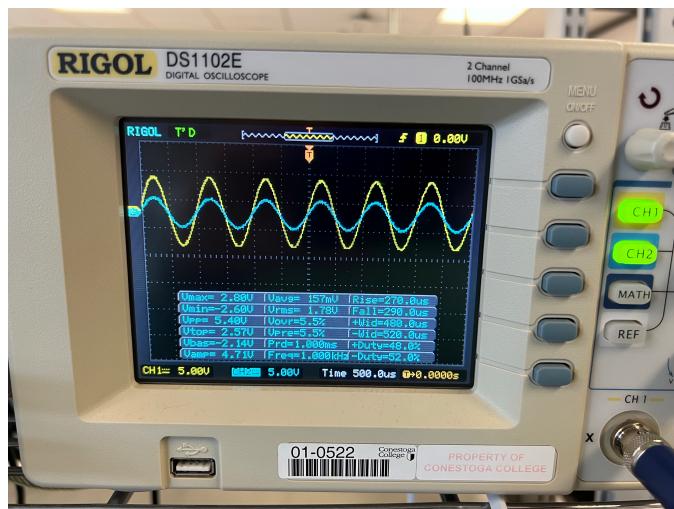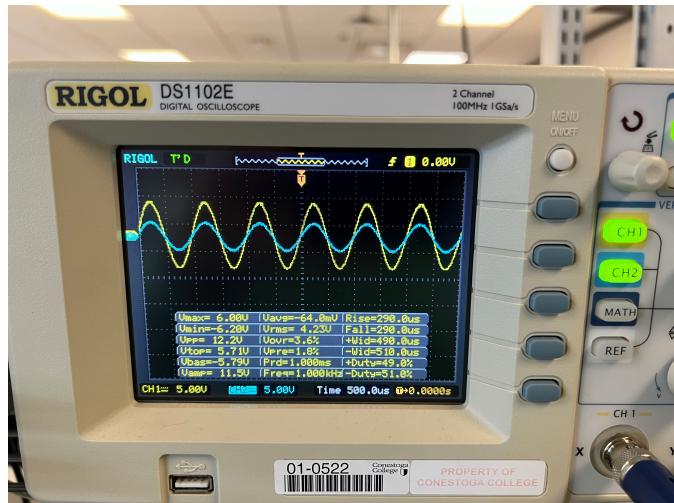

## Real Value

Type	CH1	CH2
$V_{max}$	6V	2.8V
$V_{min}$	-6.2V	-2.6V
$V_{pp}$	12.2V	5.4V



## Multisim Value

Type	CH1	CH2
Max	6V	2.5V
Min	-6V	-2.5V
Pk-Pk	12V	5V

Case 4:

CH1: 6 Vpp

CH2: 3 Vpp

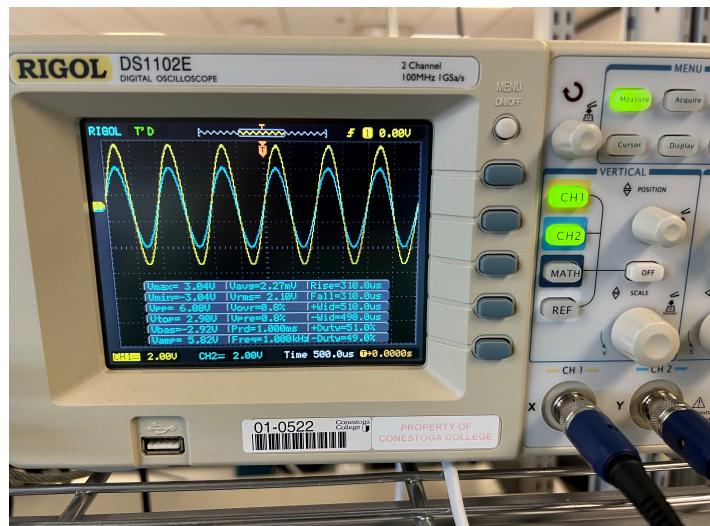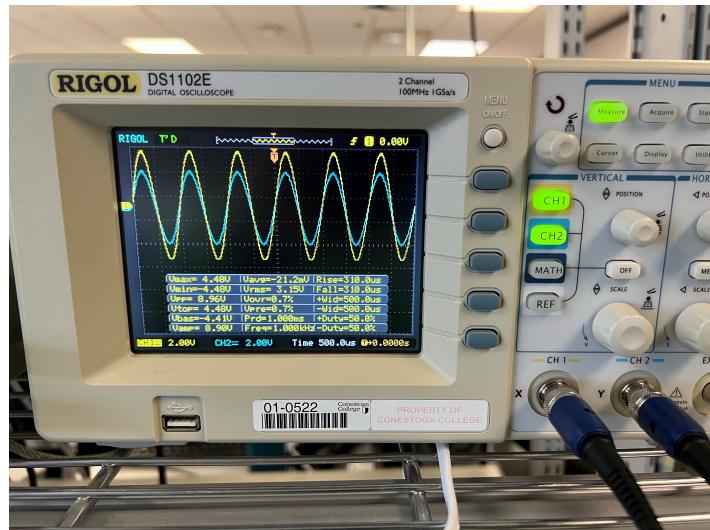

### Real Value

Type	CH1	CH2
$V_{max}$	4.48V	3.04V
$V_{min}$	-4.48V	-3.04V
$V_{pp}$	8.96V	6.08V



### Multisim Value

Type	CH1	CH2
Max	4.5V	3V
Min	-4.5V	-3V
Pk-Pk	9V	6V

### Case 5:

CH1: 6 Vpp

CH2: 4 Vpp

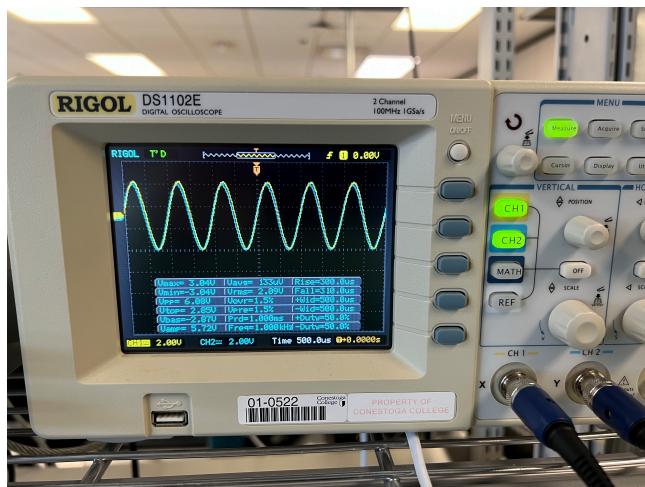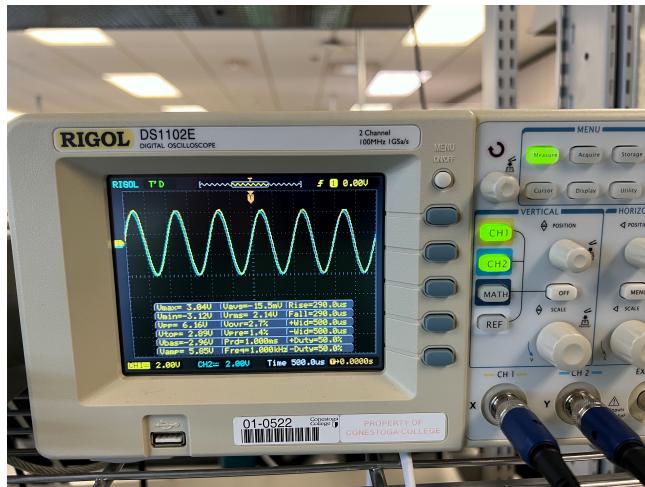

### Real Value

Type	CH1	CH2
<b>V<sub>max</sub></b>	3.04mV	3.04V
<b>V<sub>min</sub></b>	-3.12mV	-3.04V
<b>V<sub>pp</sub></b>	6.16V	6.08V

### Multisim Value

Type	CH1	CH2
<b>Max</b>	3V	3V
<b>Min</b>	-3V	-3V
<b>Pk-Pk</b>	6V	6V

### Input:

Case 1:

CH1: 2 V<sub>pp</sub>  
CH2: 1 V<sub>pp</sub>

Case 2:

CH1: 5 V<sub>pp</sub>  
CH2: 2 V<sub>pp</sub>

Case 3:

CH1: 5 V<sub>pp</sub>  
CH2: 1 V<sub>pp</sub>

Case 4:

CH1: 6 V<sub>pp</sub>  
CH2: 3 V<sub>pp</sub>

Case 5:

CH1: 6 V<sub>pp</sub>  
CH2: 4 V<sub>pp</sub>

### Observations:

From the observation we can see that the V<sub>out</sub> will be the 3 times the difference of the voltages supplied. We can also see that there is noise in the output where the values are not totally exact as the values that we get using the formula.

### Calculations:

$$A_{cl} = (1 + 2R_1/R_G)R_3/R_2 = (1 + 2(10K)/10K) * 10K/10K = (1 + 2) * 1 = 3$$

Since all resistors have the same value.

Case 1:

$$V_{out} = A_{cl} * (V_2 - V_1) = 3 (2 - 1) = 3V$$

Case 2:

$$V_{out} = A_{cl} * (V_2 - V_1) = 3 (5 - 2) = 9V$$

Case 3:

$$V_{out} = A_{cl} * (V_2 - V_1) = 3 (5 - 1) = 12V$$

Case 4:

$$V_{out} = A_{cl} * (V_2 - V_1) = 3 (6 - 3) = 9V$$

Case 5:

$$V_{out} = A_{cl} * (V_2 - V_1) = 3 (6 - 4) = 6V$$

## Theory Vs Practical:

If we look at the values from multisim and the actual values from the oscilloscope we can see that the values we get are not totally exact has the values since there is noise in the output has the values undershoot when the voltage is lower than 9 but overshoot when the voltage is around 12 V.

## Conclusions:

We can finally conclude that if the resistors have the same voltage as the rest of the circuit the instrumental amplifier will have the difference of the supplied voltages amplified by 3. Also we can conclude that with the resistance of the  $R_g$  will increase or decrease the amplification if it is changed with increasing the resistance will lower the amplification. Also decreasing the  $R_g$  value will increase the amplification of the circuit.=